

Karnaugh

Decodificador de display

a

		A_1A_0			
		00	01	11	10
A_3A_2	00	1	0	1	1
	01	0	1	1	1
	11	0	1	1	1
	10	0	1	1	0

$$\bar{A}_3\bar{A}_1 + A_2A_0 + A_2A_1 + A_3A_0 + \bar{A}_3\bar{A}_2\bar{A}_0$$

b

		A_1A_0			
		00	01	11	10
A_3A_2	00	1	0	0	0
	01	1	1	0	1
	11	1	0	0	1
	10	1	1	1	0

$$\bar{A}_1\bar{A}_0 + A_2A_1 + \bar{A}_3A_2\bar{A}_1 + A_3\bar{A}_2\bar{A}_0$$

c

		A_1A_0			
		00	01	11	10
A_3A_2	00	0	1	1	1
	01	0	0	0	1
	11	1	1	0	1
	10	1	1	0	1

$$A_1\bar{A}_0 + A_3\bar{A}_1 + \bar{A}_3\bar{A}_2A_0$$

